
CPSC 322: Introduction to Artificial Intelligence (Section 102) Logics: Botton-up proof procedures

Do this exercise in pairs. If there's an odd number, do it in a group of 3. **Submit** the sheet before leaving.

Name of Student (last, first)	Student Number

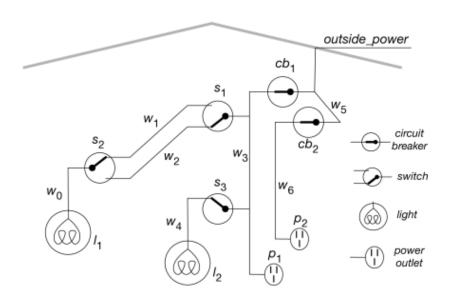

Question 1: Define relevant propositions for each of the following. (For example,)

- 1. For each wire
- 2. For each circuit breaker
- 3. For each switch
- 4. For each light
- 5. For each outlet

Question 2: How many interpretations are there?

Question 3: Suppose you are given the following knowledge base. Apply the bottom-up proof procedure to the knowledge base.

down_s ₁ .	live_l₁ ← live_w₀
<i>up_s₂.</i>	$live_{-}w_{0} \leftarrow live_{-}w_{1} \land up_{-}s_{2}.$
<i>up_s₃.</i>	$live_{-}w_{0} \leftarrow live_{-}w_{2} \land down_{-}s_{2}.$
ok_cb₁.	$live_{-}w_{1} \leftarrow live_{-}w_{3} \land up_{-}s_{1}.$
ok_cb ₂ .	$live_{-}w_{2} \leftarrow live_{-}w_{3} \land down_{-}s_{1}$
live_outside.	live_l₂ ← live_w₄.
	$live_{-}w_{4} \leftarrow live_{-}w_{3} \land up_{-}s_{3}.$
	live_p₁ ← live_w₃.
	$live_{-}w_{3} \leftarrow live_{-}w_{5} \land ok_{-}cb_{1}.$
	$live_p_2 \leftarrow live_w_6$.
	$live_{-}W_6 \leftarrow live_{-}W_5 \land ok_{-}cb_2.$
	live_w₅ ← live_outside.